
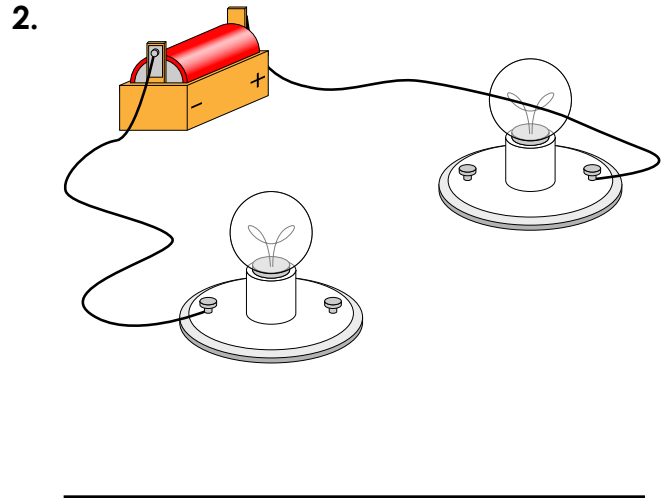


Name: _____

Electrical Circuits

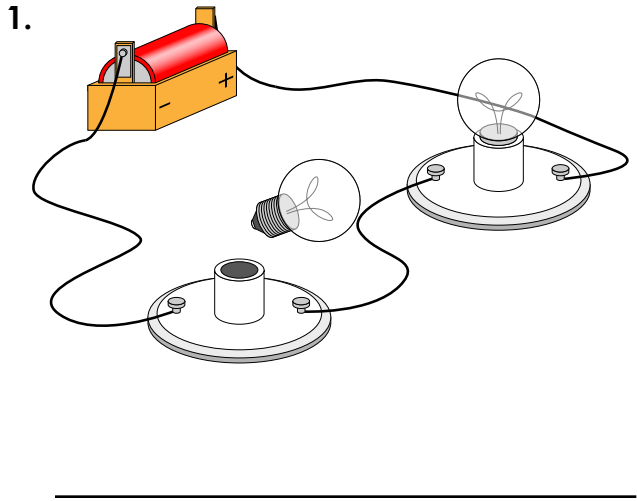Tell whether the light bulb or bulbs **will light** or **will not light** based on the circuit.





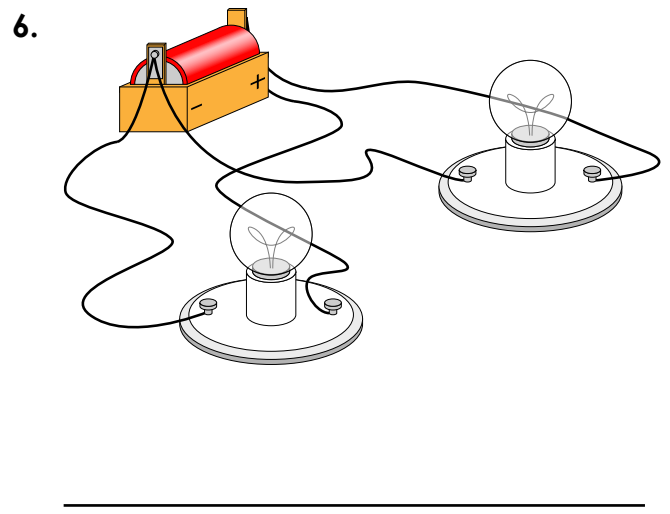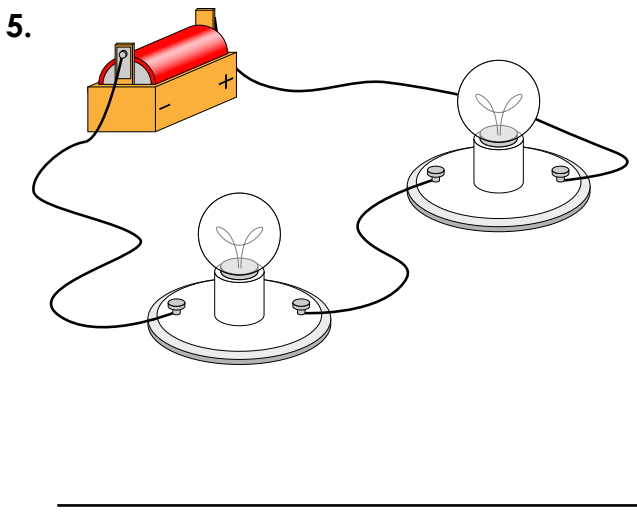3. 



PREVIEW

Please log in or register to download the printable version of this worksheet.




ANSWER KEY

Electrical Circuits


Tell whether the light bulb or bulbs will light or will not light based on the circuit.

1.

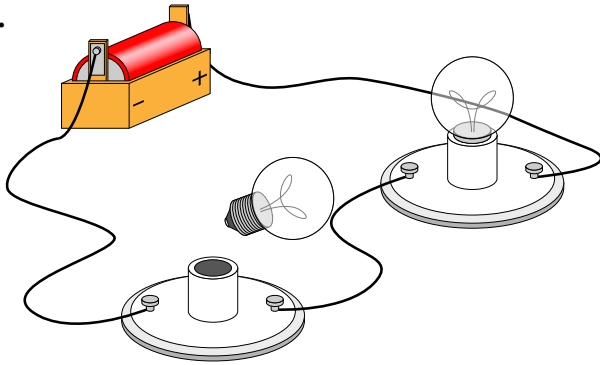

will not light

2.

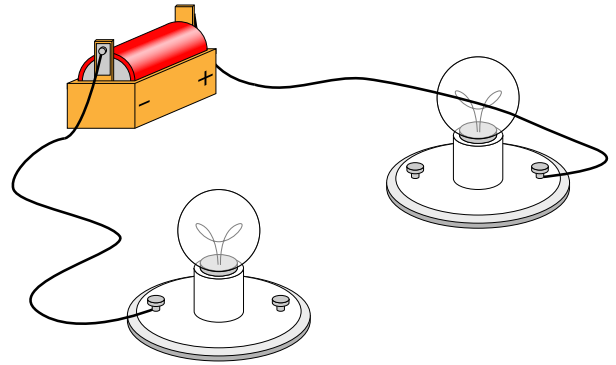

will not light


3.

PREVIEW
Please log in or register to download the printable version of this worksheet.

will light


will not light

5.

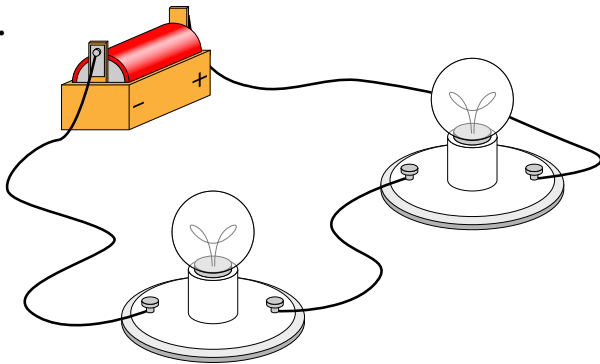

will light

6.

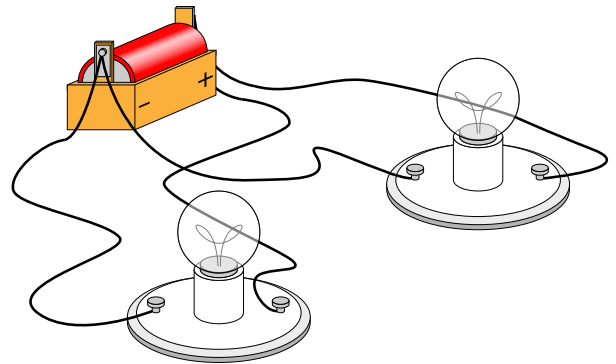

will light