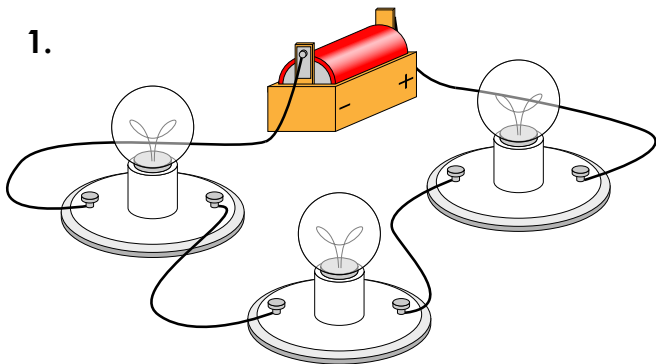


Name: _____

Series & Parallel Circuits


Tell whether each picture shows a **series circuit** or **parallel circuit**.

1.



type: _____

2.

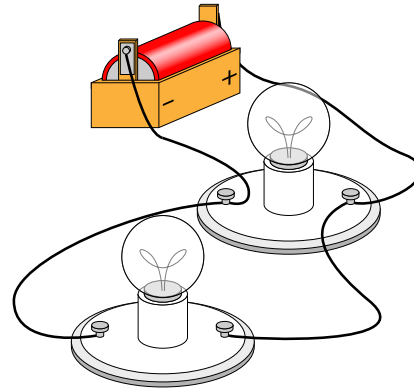

type: _____

3.




PREVIEW

Please log in or register to download the printable version of this worksheet.

type: _____


type: _____

5.

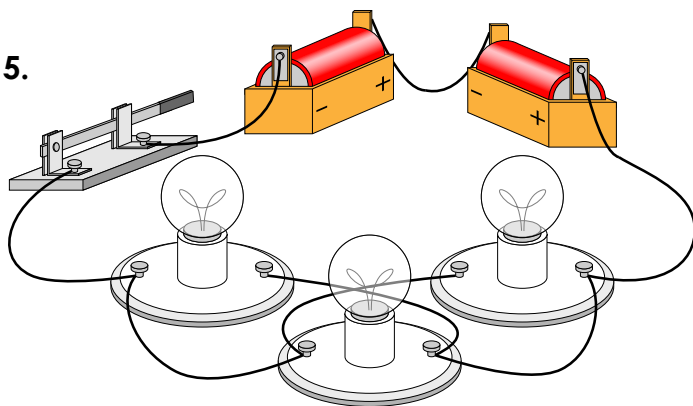

type: _____

6.

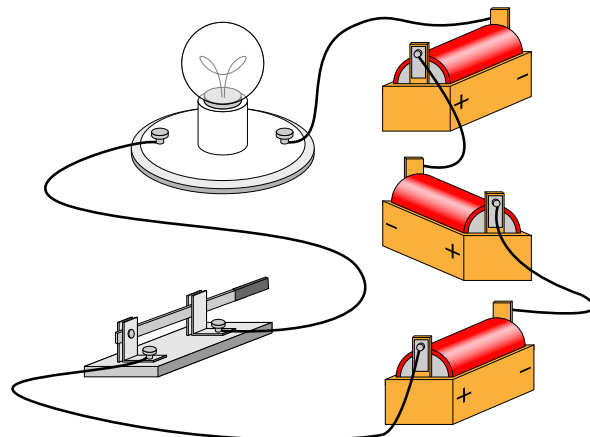


type: _____

ANSWER KEY

Series & Parallel Circuits


Tell whether each picture shows a series circuit or parallel circuit.

1.

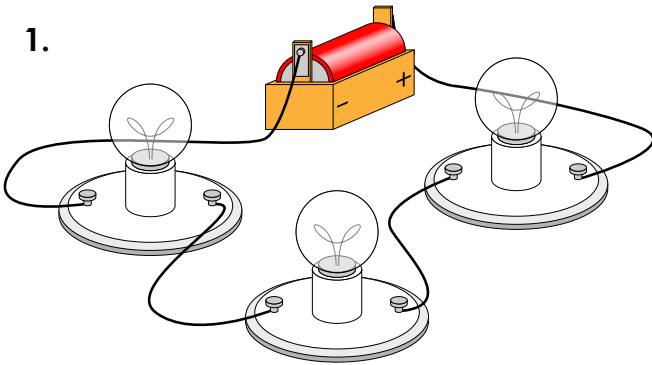

type: series circuit

2.

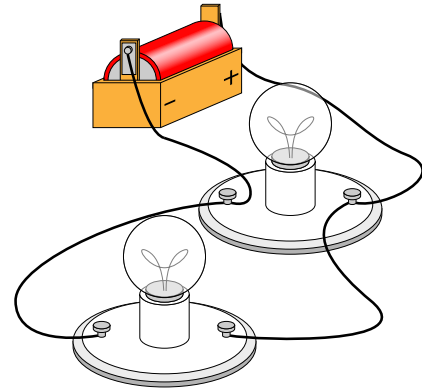

type: parallel circuit

3.




PREVIEW

Please log in or register to download the printable version of this worksheet.

type: parallel circuit


type: series circuit

5.

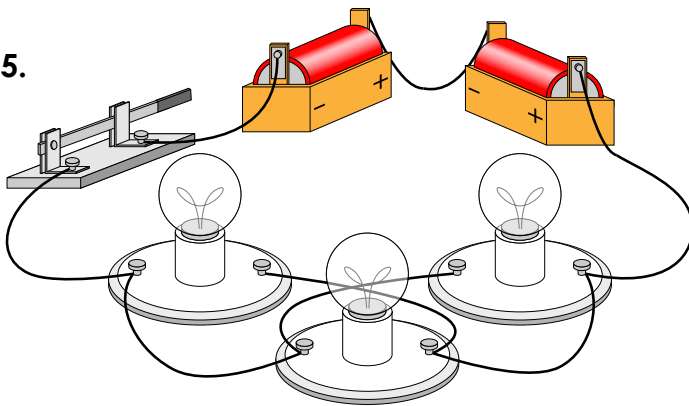

type: parallel circuit

6.

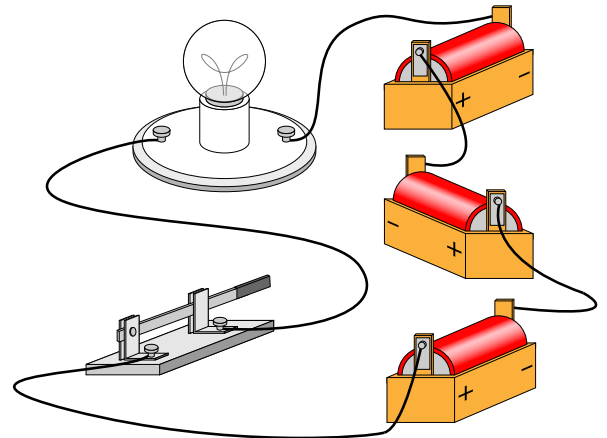

type: series circuit